



FEDERAL UNIVERSITY OF TECHNOLOGY MINNA, NIGERIA
SCHOOL OF ELECTRICAL ENGINEERING AND TECHNOLOGY
DEPARTMENT OF MECHATRONICS ENGINEERING
FIRST SEMESTER 2019/2020 ACADEMIC SESSION

MCE 531: Electronic Instrumentation and Design

TIME ALLOWED: 2 HOURS

CREDIT UNIT: 2

LEVEL: 500

Instruction: Attempt all Questions

Question 1 (25marks)

- Explain in details what you understand by: Noise, Noise flow, and characterization. In your explanation do not forget to discuss the usefulness of Noise in mechatronics system design.
- A SMT2047 Op-amp was used in the design of an audio system for Mechatronics lecture hall, the noise spectrum of the op-amp is $2.5\text{nV}/\sqrt{\text{Hz}}$ and was used over an audio frequency range of 30Hz to 50kHz, with a gain of 60dB, the output voltage was measured to be 0dBv, Calculate the Signal to Noise ratio of the design.
- With the aid of a well labelled graph, explain what you understand by Noise Corner Frequency.

Question 2 (25marks)

- Establish a signal Conditioning system using whetstone bridge to convert the change in resistance to change in voltage and derive the condition for unbalance system to show its output voltage.
- A platinum resistance temperature sensor has a resistance of 100 ohm at 0°C is placed in one arm of a Wheatstone bridge with each of the other arms also being 100ohm. If the resistance temperature coefficient of the platinum is 0.003/K. Determine output voltage from the bridge per degree change in temperature. If the load across the output can be assumed to be infinite with supply voltage of 6v.
- Differentiate between Accuracy and Precision in relation to Wheatstone bridge design.

Question 3 (25marks)

- Define the term Signal conditioning

- (b.) The difference in voltage between the emfs of the two junctions of the thermocouple is designed to amplified the output signal. If a temperature difference between the thermocouple junctions 10°C produces an emf difference of 530 microvolts.
- Draw a circuit to suit the amplification process
 - Determine the values of the resistor R_1 and R_2 assuming the circuit gives out 10mv at the output.
- (c.) If an RC low pass filter with a resistor of 1Kohm and a capacitor 47nF has been designed by a student form the Department of Mechatronics Engineering for laboratory use. Draw a likely circuit diagram for such a design and determine its cutoff frequency.

Question 4 (25marks)

- Define the term Data Acquisition system and mention the primary function of Analogue to Digital Cs Converter (ADC) as a parameter in a typical data acquisition system (DAQ)
- A simple DAQ system block consists of a switching network (multiplexer), an instrumentation amplifier and an analog-to-digital converter (ADC). Draw the circuit or block diagram to implement it.
- Enumerate 3(three) ways in which data acquisition system differs from other measuring instrument like voltmeter.