

**Federal University of Technology Minna**  
**School of Technology Education**  
**Industrial and Technology Education Department**

First Semester Examination, 2012/2013 Session


Course: - Circuit Theory (IET 313)

Duration:- 2 hours.


Instruction:- Answer all Questions in Section A and any two Questions from Section B

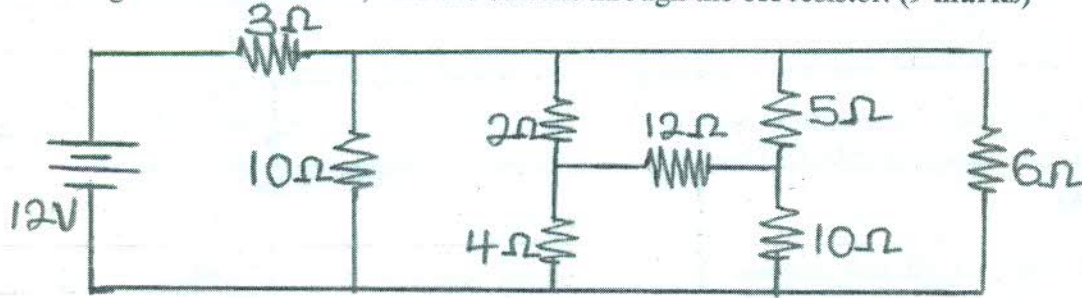**Section A**


1a. Using Norton's theorem, find the current through the  $6\Omega$  resistor. (9 marks)



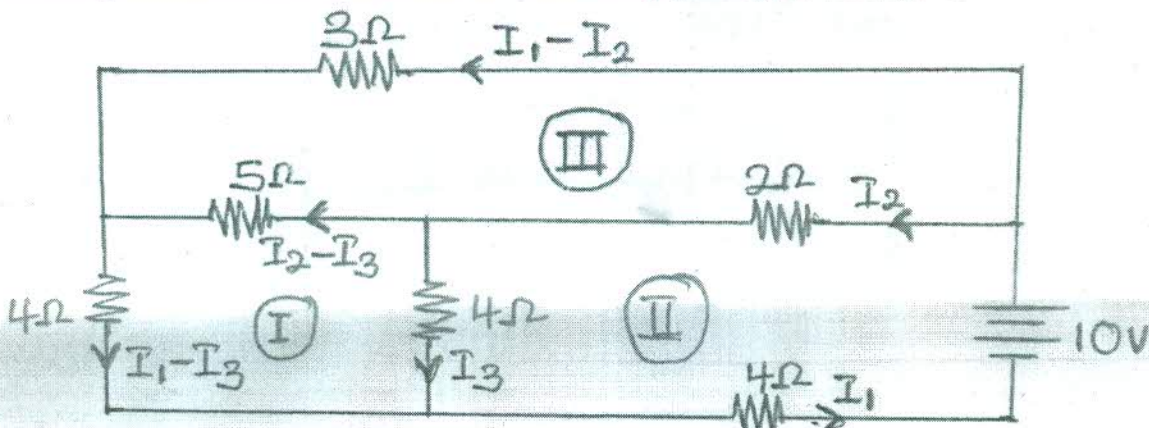
1b. Using Kirchhoff's laws calculate the currents  $I_1$ ,  $I_2$  and  $I_3$  (11 marks)



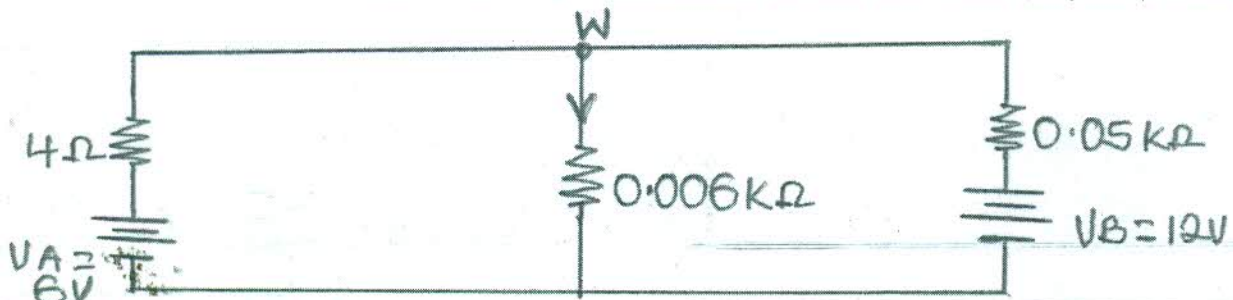2a. Determine the value of  $I_1$ ,  $I_2$  and  $I_3$  using Superposition theorem and Nodal analysis. (14 marks)



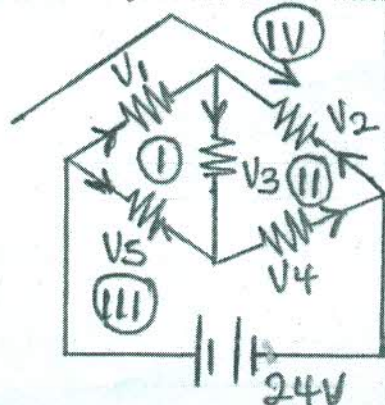
2b. Find the value of  $V_1$ ,  $V_4$  and  $V_5$  for the circuit when  $V_2 = 8V$  and  $V_3 = 6V$  (6 marks)


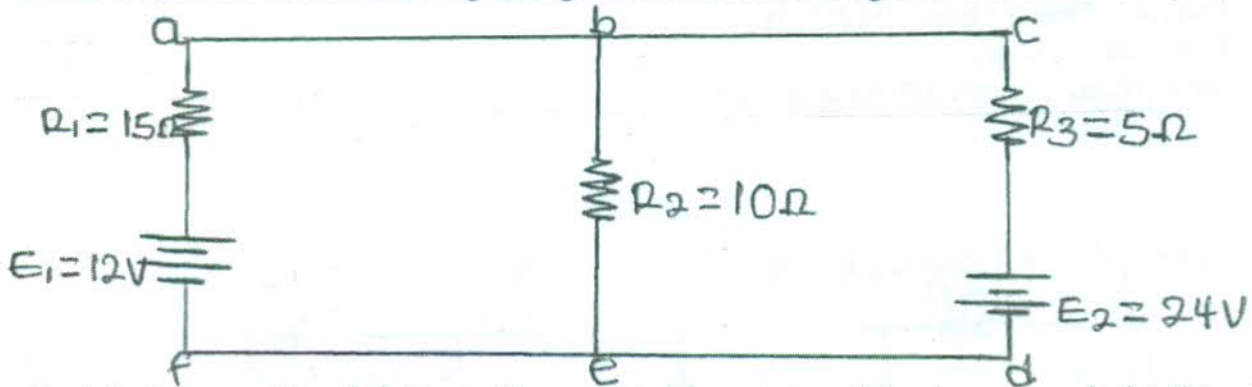
## Section B


3a. With the aid of diagram shows the classification of electrical network and explain each term. (10 marks)

4a. Determine the current  $I$  flowing through the  $10\Omega$  resistor using Thevenin's theorem. (7 marks)



4b. A battery consists of sixteen cells connected in series, each having an e.m.f of  $1.5V$  and the internal resistance of  $0.15\Omega$ . Calculate the maximum power transferred to an external load. (3 marks)

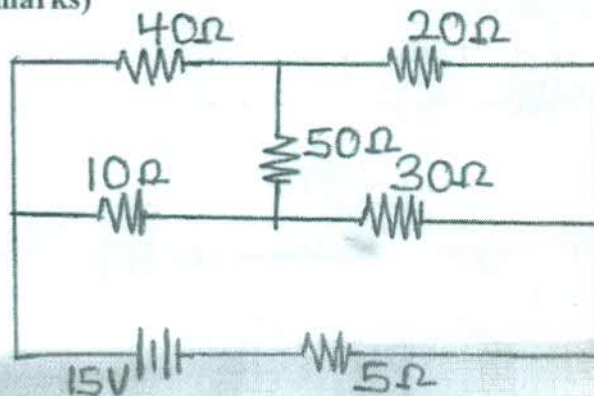5a. In the network shown below, find the current supplied by the battery using star/delta transformation. (7 marks)



5b. Define Thevenin's voltage and Thevenin's resistance. (3 marks)